 


Shakespeare be
like...



EECS 370 - Lecture 9

Sequential Logic

Poll: What is
NOR(0,X)?



Announcements

- Project 2 posted
 - First part due next Thursday
- HW 1 due yesterday
 - Can still submit by tonight for reduced credit
 - HW 2 posted later this week
- First exam 2.5 weeks from today
 - Covers up through next week's lectures ("Multi-cycle" is last topic)
 - Recommend reviewing earlier material now
 - Rework through previous lab problems
 - Sample exams available on website
 - AI tools have decent hit rate at generating simple questions

My OH Adjustments





- I have a new office!
 - My OH will be in 4812 BBB going forward
- One time only change:
 - This Thursday (9/25) OH pushed to 3-4 pm

Next few lectures: Digital Logic

- Lectures 1-7:
 - LC2K and ARMv8/LEGV8 ISAs
 - Converting C to Assembly
 - Function Calls
 - Linking
- Lecture 8:
 - Finish up linking
 - Combinational Logic
- **Today:**
 - **Continue combinational logic**
 - **Sequential Logic**



Review

    


Building Complexity: Selecting

- We want to design a circuit that can select between two inputs (multiplexer or **mux**)
- Let's do a one-bit version
 1. Draw a truth table

A	B	S	O
0	0	0	
0	0	1	
0	1	0	
0	1	1	
1	0	0	
1	0	1	
1	1	0	
1	1	1	

Symbol

 

$$O = S ? B : A$$




Building Complexity: Selecting

- We want to design a circuit that can select between two inputs (multiplexor or **mux**)
- Let's do a one-bit version
 1. Draw a truth table


Muxes are universal! A 2^N entry truth table can be implemented by passing each output value into an input of a 2^N -to-1 mux

A	B	S	O
0	0	0	0
0	0	1	0
0	1	0	0
0	1	1	1
1	0	0	1
1	0	1	0
1	1	0	1
1	1	1	1

Circuit

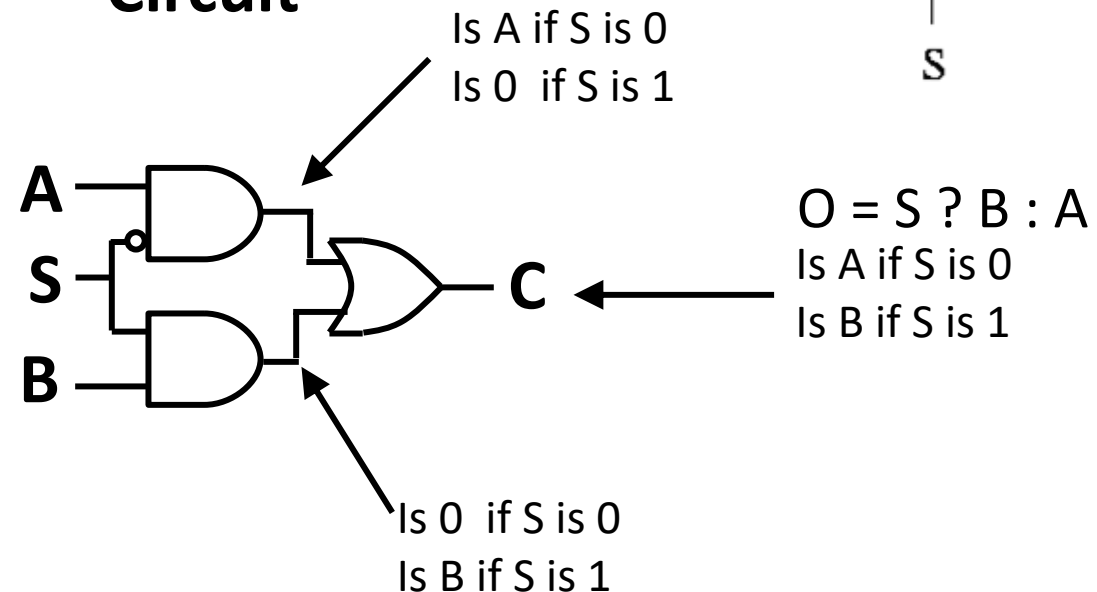


Symbol

 

Building Complexity: Decoding

- Another common device is a decoder
 - Input: N-bit binary number
 - Output: 2^N bits, exactly one of which will be high
 - Allows us to **index** into things (like a register file)

Decoder

 

Poll: What will be the output for 101?

Building Complexity: Addition

- We want to design a circuit that performs binary addition
- Let's start by adding two bits
 - Design a circuit that takes two bits (**A** and **B**) as input
 - Generates a sum and carry bit (S and C)
 1. Make a truth table
 2. Design a circuit


$$\begin{array}{r} 10011 \\ + 00110 \\ \hline \end{array}$$

A	B	C	S

Building Complexity: Addition

- We want to design a circuit that performs binary addition
- Let's start by adding two bits
 - Design a circuit that takes two bits (**A** and **B**) as input
 - Generates a sum and carry bit (S and C)
 - 1. Make a truth table
 - 2. Design a circuit

 
$$\begin{array}{r} 0\ 1\ 1\ 0 \\ 1\ 0\ 0\ 1\ 1 \\ + 0\ 0\ 1\ 1\ 0 \\ \hline 1\ 1\ 0\ 0\ 1 \end{array}$$



A	B	C	S
0	0	0	0
0	1	0	1
1	0	0	1
1	1	1	0

Building Complexity: Addition

 - Now we can add two bits, but how do we deal with carry bits?
- This is a **full adder**
 - We have to design a circuit that can add three bits
 - Inputs: A, B, C_{in}
 - Outputs: S, C_{out}
- 1. Design a truth table
- 2. Circuit
- This is a **full adder**




$$\begin{array}{r} 0110 \\ 10011 \\ + 00110 \\ \hline 11001 \end{array}$$

C _{in}	A	B	C _{out}	S
0	0	0	0	0
0	0	1	0	1
0	1	0	0	1
0	1	1	1	0
1	0	0	0	1
1	0	1	1	0
1	1	0	1	0
1	1	1	1	1

8-bit Ripple Carry Adder

 
If we invert B's bits and set C to 1, we also have a subtractor! Why?




This will be very slow for 32 or 64 bit adds, but is sufficient for our needs

Propagation delay in combinational gates

 - Gate outputs do not change exactly when inputs do.
 - Transmission time over wires (\sim speed of light)
 - Saturation time to make transistor gate switch
- ⇒ Every combinatorial circuit has a propagation delay
(time between input and output stabilization)



Timing in Combinational Circuits

 


What is the input/output delay (or simply, delay) of the MUX?

What is the delay of this Circuit?

Each oval represents one gate,
the type does not matter



Poll : What is the delay?

 

We only care about the longest
path, or critical path

  
Exercise

- Use the blocks we have learned about so far (full adder, NOR, mux) to build this circuit
 - Input A, 32 bits
 - Input B, 32 bits
 - Input S, 1 bit
 - Output, 32 bits
 - When S is low, the output is $A+B$, when S is high, the output is $\text{NOR}(a,b)$
- Hint: you can express multi-bit gates like this:



 Exercise

- This is a basic ALU (Arithmetic Logic Unit)
- It is the heart of a computer processor!




Sequential Logic

- Can we build a processor out of these combinational elements?
- How to build something like a program counter (PC)?
 - Increment it for every instruction... fine, use an adder
 - But only increment it once ready to move on to next instruction
 - That takes a finite amount of time... until then we need to "remember" the current value
- Combinational logic's output is determined from current input
 - But computers have "state" – they remember previous inputs and behave differently based on its history

Sequential Logic

- Examples of state
 - Registers
 - Memory
 - PC
- Sequential logic's output depends not only on current input, but also the current state
- This lecture will show you how to build sequential logic from gates
 - Key is feedback



Using feedback to "remember"

 

- This remembers its initial value!
- Very basic memory
- What's wrong with this, though?


Let's look at the following circuit

  Useful identify:
 $\text{NOR}(0, X) = \text{NOT}(X)$




S	R	Q	\bar{Q}
0	0	Q	\bar{Q}

 When $R=S=0$, turns
into our memory
element!




Let's look at the following circuit

 

S	R	Q	\bar{Q}
0	0	Q	Q
0	1	0	1

What is the value of Q if R is 1 and S is 0?

Let's look at the following circuit

 


S	R	Q	\bar{Q}
0	0	Q	Q
0	1	0	1
1	0	1	0

What is the value of Q if R is 0 and S is 1?

SR Latch

 - So this circuit (an SR latch):
 - "Sets" Q to 1 when $S=1$ $R=0$
 - "Resets" Q to 0 when $S=0$ $R=1$
 - "Latches" Q when $S=0$ $R=0$
 - What about when $S=1$ $R=1$?




S	R	Q	\bar{Q}
0	0	Q	\bar{Q}
0	1	0	1
1	0	1	0
1	1	0	0

BAD! Why?

SR Latch – Undefined behavior

 
- If $S=1$, $R=1$, then Q and its inverse are both 0
- If inputs then change to $S=0$, $R=0$, we get this circuit




- This is unstable! Output rapidly oscillates between 0 and 1

Improving SR Latch

 - SR Latch works great at saving a bit of data...
 - Unless $S=R=1$, even for a fraction of a second
- Idea: let's prevent that from happening by adding AND gates in front of each input
 - Impossible for R and S to both be 1




Transparent D Latch

 

Next state is set

D	G	Q	\bar{Q}
0	0	Q	\bar{Q}
0	1	0	1
1	0	Q	\bar{Q}
1	1	1	0

Set state
is retained
when gate
is low

 

No invalid
states 😊


Transparent D Latch

- When G ("gate") is high, $Q=D$ (the latch is "transparent")
- When G is low, Q "latches" to the value of D at that instant and remembers, even if D changes later


D	G	Q	\bar{Q}
0	0	Q	\bar{Q}
0	1	0	1
1	0	Q	\bar{Q}
1	1	1	0

Next state is set


Set state is retained when gate is low

 

D-Latch Timing Diagram

 


D-Latch Timing Diagram

 


Is D-Latch Sufficient?

 - Can we use D-latches to build our PC logic?
- Idea:
 - Use 32 latches to hold current PC, send output Q to memory
 - Also pass output Q into 32-bit adder to increment by 1 (for word-addressable system)
 - Wrap sum around back into D as "next PC"
 - Once ready to execute next instruction, set G high to update



Shortcoming of D-Latch

 
- Problem: G must be set very precisely
 - Set high for too short: latch doesn't have enough time for feedback to stabilize
 - Set high for too long: Signal may propagate round twice and increment PC by 2 (or more)
- Challenging to design circuits with exactly the right durations




Not just a problem for PC, much of our processor will involve logic like this

Adding a Clock to the Mix

 - We can solve this if we introduce a **clock**
 - Alternating signal that switches between 0 and 1 states at a fixed frequency (e.g., 1 GHz)
 - Only store the value the **instant** the clock changes (i.e. the **edge**)



Adding a Clock to the Mix

 


We won't discuss it further here, but this circuit sets $Q=D$ **ONLY** when clock transitions from 0 -> 1


Intuitively, the design works by inverting the Gate signals, so only one passes at a time (like a double set of sliding doors)



D Flip-Flop Timing Diagram

 


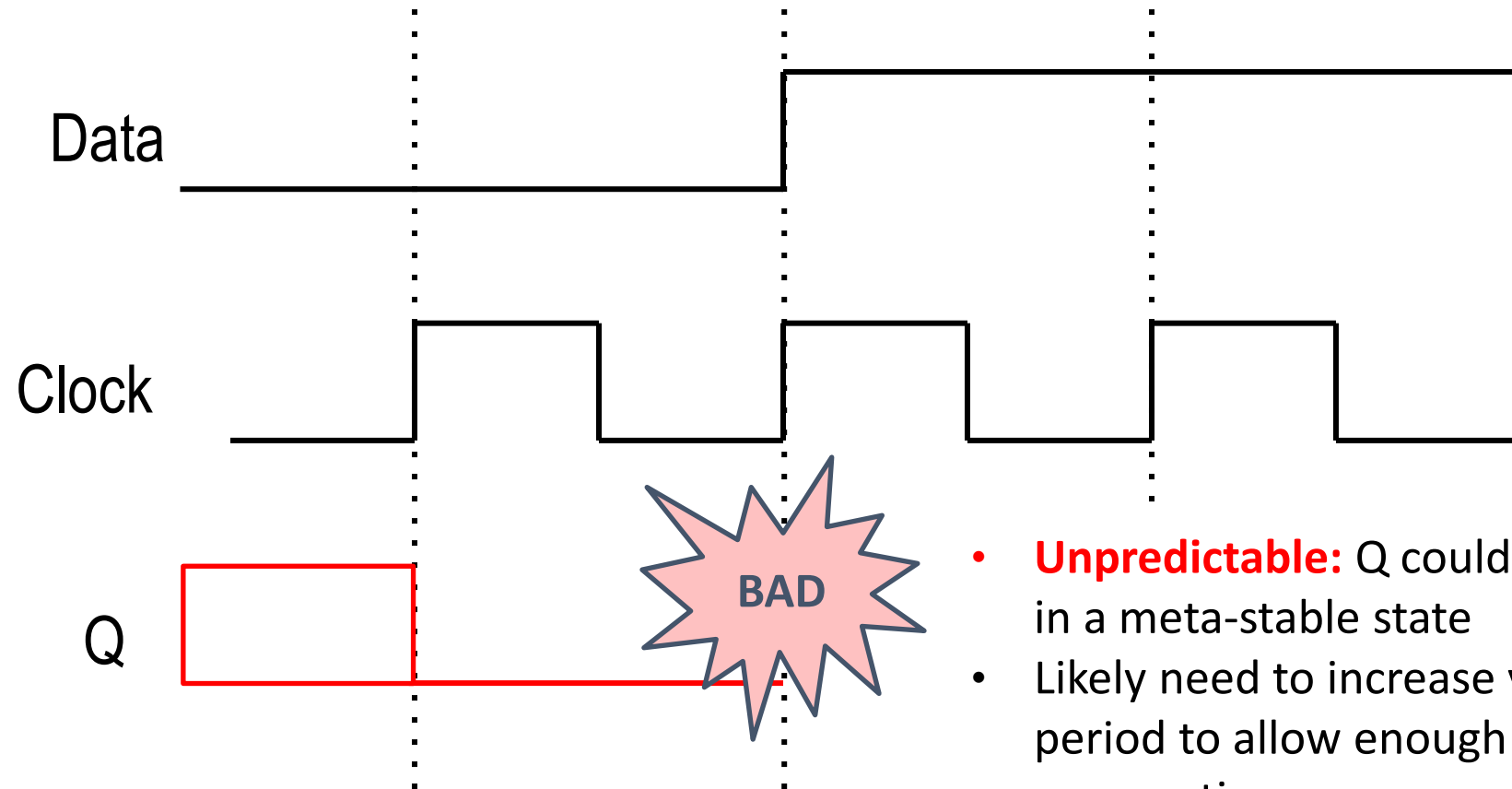What happens if Data changes on clock edge?




- **Unpredictable:** Q could be high, low or in a meta-stable state
- Likely need to increase your clock period to allow enough time for signal propagation


Latches vs Flip-flops

 

D Latch

 


D Flip-flop

 

Enabled D Flip-flop
(only updates on
clock edge if 'en' is
high)

Next Time

- Finite State Machines
- Introduce first processor implementation

Me: Mom, can I have  ?

Mom: No we have  at home

